Ciarcia's Circuit Cellar

Copyright @ 1980 by Steven A Ciarcia. All rights reserved

I/O Expansion for the TRS-80

Part 2: Serial Ports

Steve Ciarcia POB 582 Glastonbury CT 06033

Last month in Part 1, I discussed the attachment of parallel input and output ports to the Radio Shack TRS-80 computer. This was basically a response to the many inquiries I have had on TRS-80 interfacing. As usual, it was a general presentation, intended to first enlighten the reader with interfacing concepts and then tender a few alternative circuits for construction. While TRS-80 owners benefit most directly, many computers have similar bus structure and can just as easily accommodate parallel input/output (I/O) expansion.

The presentation this month of a serial interface for the TRS-80 required a little more thought. Parallel ports are strictly hardware devices which in their simplest form only require execution of a single assemblylanguage or BASIC instruction to function efficiently. A serial interface, on the other hand, needs a software program to direct its operation. The many registers and buffers involved in the serial communication process must be synchronized by the execution of a serial-driver routine stored in memory. Any design for a serial port has to take into account the capabilities and memory location of this routine. Even the most splendid hardware circuit would be a failure if the software driver interfered with other computer functions.

To eliminate any potential problems that might occur, I decided to make my design completely softwarecompatible with existing TRS-80 serial-driver routines. This does not necessarily minimize circuit complexity by any means, but it greatly enhances potential user acceptance.

I was equally concerned with the power requirements and physical

This RS-232C interface design is compatible with existing TRS-80 serial-interface control software.

configuration. Radio Shack sells a serial-interface board for the TRS-80, but it cannot be operated independently and requires integral attachment to the expansion interface

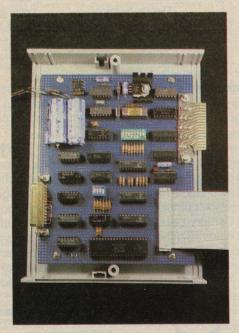


Photo 1: Prototype of the COMM-80 interface. The ribbon cable at the lower right connects to the expansion-bus port (either the expansion connector on the keyboard/processor unit or connector J2 on the expansion interface). The edge connector at the upper right is for the Centronics-compatible, parallel printer port. The RS-232C DB-25S connector is at the lower left.

module. The expansion interface and one serial port add \$400 to the cost of the basic computer. Also, with its present hardwired addressing, the TRS-80 can support only one serial port and one parallel printer port.

Depending upon the intended application, you may not need the extra functions (eg: disk controller and memory expansion) provided in the expansion interface. The \$300 outlay for the expansion interface is an extraordinary expense if you merely intend to attach a modem and use the TRS-80 as a terminal on a timesharing network, such as the Source or MicroNet. Rather than duplicate what I consider to be a restrictive hardware configuration, I have attempted to present a cost-effective communications interface that gives more flexibility in use and has a better price/performance ratio.

The COMM-80 Communications Interface

The approach I decided to take was to combine elements from Part 1 of this article with this one, and produce a stand-alone serial/parallel interface which could plug directly into the expansion-bus connector (the keyboard-unit expansion connector or connector J2 on the expansion interface). Designated the COMM-80, the unit includes a 50 to 19,200 bit per second (bps) RS-232C serial port, a full 8-bit-in/8-bit-out parallel printer port, an auxiliary expansion-port edge connector, and switch-selectable addressing which allows a single TRS-80 to simultaneously connect up to sixteen COMM-80 interfaces. A block diagram of the COMM-80 is presented in figure 1, and a picture of the prototype is in photo 1.

What Is a Serial Port?

Communication between computers, terminals, and other peripheral devices can be in either serial or parallel mode. In parallel mode, the entire information segment (ie: data word) is transmitted or received simultaneously in a single time frame. In serial mode, this same information is divided into its constit-

uent bits and these bits are transmitted individually over a longer period of time. In cases where high-speed data rates are involved, such as in interaction with a floppy-disk drive, the communication is usually in parallel and can involve as many as forty data and control lines. Serial mode is generally used for lower-speed exchanges.



Photo 2: Here are two ways of adding RS-232 communication capability to the Radio Shack TRS-80. The COMM-80 unit is shown on the left; the combination of the Radio Shack expansion interface and serial-interface board is shown on the right.



Photo 3: A TRS-80 equipped with Level II BASIC, the COMM-80 interface, and a Novation CAT modem can be used as a remote terminal for a time-sharing service such as the Source.

An example a little closer to home is the addition of a video terminal and a printer to a computer system. Both the terminal and printer are designed to accept American Standard Code for Information Interchange (ASCII) coding, which requires only 7 bits to define a character.

The connections between the computer and the video terminal can be either serial or parallel. The choice in this case is not determined by data rate but by expense. Parallel communication is relatively easy and inexpensive for a computer. Few components are involved, and a 6-foot length of nine-conductor cable (seven lines to carry the 7-bit ASCII data, one line each for data strobe and ground) will not cost too much. Serial interfacing is another matter entirely.

Microprocessors do not naturally communicate in serial format. There are no single machine-language instructions to perform this function. To serialize data we must add a separate hardware device called a universal asynchronous receiver/transmitter (UART). It looks just like a parallel port to the processor, but internally the UART is a very complicated device.

A UART is a special large-scale integration (LSI) circuit that accepts a data byte in parallel form from the processor and converts it into a universally accepted serial format. Any two terminals set at the same data-transmission rate could conceivably be interconnected to communicate, regardless of internal operating-system differences. The expense for this flexibility is in the neighborhood of \$200 to \$500 per data channel, depending upon the computer bus configuration.

Transmitting Serial Data

Serial data can be transmitted in either synchronous or asynchronous format. I will address this discussion only to the latter format since asynchronous communication is the technique employed in the COMM-80. The asynchronous format allows unlimited time gaps to occur between transmission of characters.

The internal structure of a UART consists of a separate parallel-to-serial transmitter and a serial-to-parallel receiver joined by common programming pins. The two sections can be used independently provided

they adhere to the same bit-format options. Sending a character from the processor is simply a matter of performing a parallel-output operation to the UART. The decoded-output strobe loads the UART with the data and initiates the serialization process.

Figure 2 shows a plot of logic levels versus time during the transmission of a single character. When no data is being sent, the data-transmission line remains in a logic 1 state. A 1-to-0 high-to-low transition on the line signifies that a character is being sent. The first bit is called a *start bit*. The

next 5 to 8 bits are data; these are followed by a parity bit. Finally, the end of transmission is defined by the addition of 1 or 2 stop bits at the end of the character. The start, stop, and parity bits are all added as part of the UART's function.

Meanwhile, the receiver section of the UART is continuously monitoring the input line for the start bit of a character. When the start bit comes, the following data bits are placed into a holding register and their parity is checked against the state of the parity bit. Completion is signaled by setting a data-available flag. This flag, plus others defining buffer status, parity, and overrun errors, is read by the processor to determine when input data is ready or when another character can be transmitted. The individual pin functions of a typical UART are described in table 1.

RS-232C Interface Characteristics

So far, I have discussed only serialization of the data. I have said nothing about voltages or logic conventions associated with control of the information transmitted between

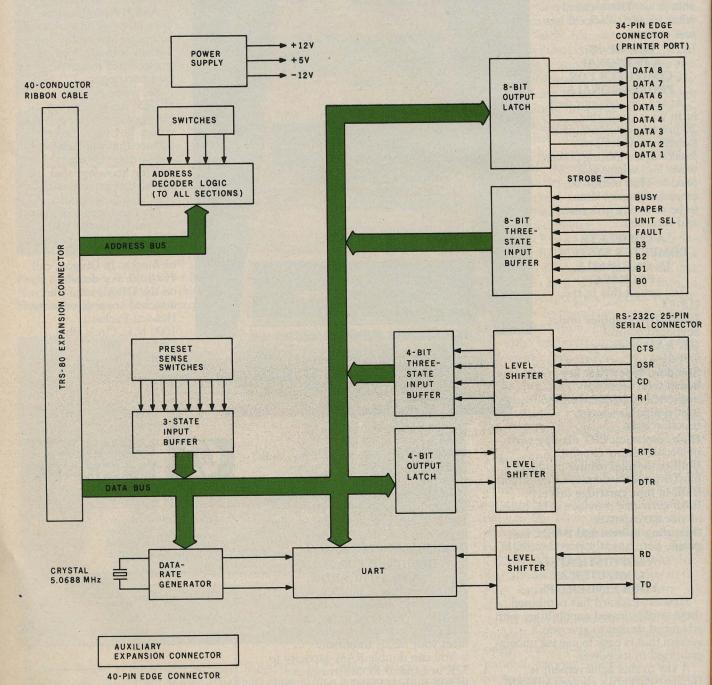


Figure 1: Block diagram of components and data flow in the COMM-80 serial and parallel interface for the Radio Shack TRS-80.

equipment. The Electronic Industry Association (EIA) RS-232C electrical specification defines voltage levels and control signals: a logic level 1 is called a "mark" or "off" and is considered to be anything more negative than -3 V. A logic 0 is called a "space" or "on" and is considered to be anything more positive than +3 V. As a rule, designers tend to use +12 V and -12 V for the 0 and 1 logic states.

In addition to standardizing the serial format, the EIA also specifies that the connector for RS-232C be a 25-pin, D subminiature type (called a *DB-25*). The pin assignments and functions are shown in table 2.

The COMM-80 Hardware

The COMM-80 is driven only by signals present on the buses of the computer. All sections communicate with the processor as memorymapped or directly addressed input/output ports. Figure 3 illustrates the complete schematic diagram of the COMM-80 interface in three sections.

There are two major sections: parallel printer port and serial port. They are joined together by a common address-decoding circuit and power supply.

Address Decoding

A standard TRS-80 expansion interface has an edge connector commonly called the Centronics printer port. It actually combines an 8-bit parallel output port and a 4-bit parallel input port. The addressing for this section is hardwired for hexadecimal memory location 37E8. Part of this same address decoder is used for the Radio Shack serial-interface board. Coincidentally, the Radio Shack serial interface is decoded to use I/O port addresses E8 thru EB for data-transfer and control functions.

The address-decoding section of the COMM-80, consisting of IC1 thru IC7, is designed to decode this set of

Pin Number	Name	Symbol	Function
1 2	V _{cc} Power Supply V _{cc} Power Supply	V_{cc} V_{gg}	+5 V Supply -12 V Supply (Not connected on AY-5-1015
3 4	Ground Received Data Enable	V _{GZ} RDE	Ground A logic 0 on the receiver-enable line places the received data onto the output
5 6 7 8 9 10 11 12	Received Data Bits	RD8 RD7 RD6 RD5 RD4 RD3 RD2 RD1	lines. These are the eight data output lines. Received characters are right justified; the least significant bit (LSB) always appears on RD1. These lines have three-state outputs.
13	Parity Error	PE	This three-state line goes to a logic 1 if the received-character parity does not agree with the selected parity.
14	Framing Error	FE	This three-state line goes to a logic 1 if the received character has no valid stop bit.
15	Over-Run	OR	This three-state line goes to a logic 1 if the previously received character is not read (DAV line not reset) before the present character is transferred to the receiver-holding register.
16	Status Word Enable	SWE	A logic 0 on this three-state line places the status word bits (PE, FE, OP, DAV, TBMT) onto the output lines.
17	Receiver Clock	RCP	This line will contain a clock whose frequency is sixteen times the desired receiver data rate.
18 18 19	Reset Data Available Data Available	RDAV DAV	A logic 0 will reset the DAV line. This three-state line goes to a logic 1 when an entire character has been re- ceived and transferred to the receiver holding register.
20	Serial Input	SI	This line accepts the serial bit input stream. A marking (logic 1) to spacing (logic 0) transition is required for initiation of data reception.
21	External Reset	XR	Resets shift registers. Sets SO, EOC, and TBMT to a logic 1. Resets DAV, and error flags to 0. Clears input data buffer. Must be tied to logic 0 when not in use.
22	Transmitter Buffer Empty	ТВМТ	The three-state transmitter buffer-empty flag goes to a logic 1 when the data bits holding register may be loaded with another character.

Table 1: Pin functions for the AY-5-1013, AY-5-1015, or COM2017 UARTs.

addresses as well as a range of other addresses. The range for the printer port is hexadecimal memory addresses 3708 to 37F8, and the serial range is hexadecimal I/O addresses 08 to F8. Figure 4 illustrates the switch settings for the different ranges.

There is a particular rationale for setting up the addresses this way. A user attaching a COMM-80 to his system would naturally set the switches for the range E8 thru EB, and the interface would then be completely compatible with standard TRS-80 software. Should an expansion-

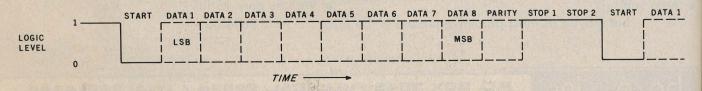


Figure 2: Logic levels plotted against time during the transmission of an 8-bit data word in asynchronous serial format.

Pin Number	Name	Symbol	Function
23	Data Strobe	DS	A strobe on this line will enter the data bits into the data-bits-holding register. Initial data transmission is initiated by the rising edge of DS. Data must be stable
24	End of Character	EOC	during entire strobe. This line goes to a logic 1 each time a full character has been transmitted. It remains at this level until the start of
25	Serial Output	SO	transmission of the next character. The entire character is transmitted bit by bit (that is, serially) over this line. It will remain at logic 1 when no data is being transmitted.
26 27 28		TD1 TD2 TD3	There are up to 8 data-bit-input lines available.
29 30 31 32 33	Data Bit Inputs	TD4 TD5 TD6 TD7 TD8	
34	Control Strobe	CS	A logic 1 on this lead will enter the control bits (EPS, NB1, NB2, TSB, NP) into the control-bits-holding register. This line can be strobed or hardwired to a logic 1 level.
35	No Parity	NP	A logic 1 on this lead will eliminate the parity bit from the transmitted and received character (no PE indication). The stop bit(s) will immediately follow the last data bit. If not used, this lead must be tied
36	Number of Stop Bits	TSB	to a logic 0. This lead will select the number of stop bits (1 or 2) to be appended immediately after the parity bit. A logic 0 will insert 2 stop bits.
37 38	Number of Bits Per Character	NB2 NB1	These two leads will be internally decoded to select either 5, 6, 7, or 8 data bits per character. NB2 NB1 bits/character 0 0 5 0 1 6 1 0 7 1 1 8
39	Odd/Even Parity Select	EPS	The logic level on this pin selects the type of parity which will be appended immediately after the data bits. It also determines the parity that will be checked by the receiver. A logic 0 will insert odd parity and a logic 1 will insert odd parity.
40	Transmitter Clock	TCP	ty, and a logic 1 will insert even parity. This line will contain a clock whose frequency is sixteen times the desired transmitter data rate.

interface module be added to the system later, the user would merely flip a switch specified by table 3 to change the port address (the expansion interface is set only for 37E8). The switch circuit is shown in figure 4. The system could then accommodate two printers. As table 3 shows, there are sixteen possibilities, so there could be sixteen printers and sixteen serial ports. From this point on, however, I will refer only to the addressing range of E8 thru EB.

The Printer Port Is a Full 8 Bits

Since I explained parallel ports in detail last month, I will discuss the

printer port briefly. Initially my intention was to provide a generalpurpose I/O port so that the user could connect some of my other projects and interface designs. As it worked out, however, I decided to combine efforts and configure the parallel port to serve as the printer port as well. The major difference is that the COMM-80 incorporates a full 8-bit input and a full 8-bit output port. Its address is nominally hexadecimal 37E8 in memory-address space. Writing to memory location 37E8 latches data onto IC14 and IC15 (both 74LS75 devices), and reading memory location 37E8 gates the

Once you have installed an RS-232 port, a whole new world of peripherals opens up.

printer status signals through the three-state buffer IC19 (a 74LS244 device).

Serial Port

The serial-port section requires four input and four output strobes to operate. As previously mentioned, the serial-port control addresses are nominally set for hexadecimal E8 thru EB. Figure 5 more explicitly illustrates the hardware derivation of these signals and lists their functions. These strobe signals coordinate the RS-232C handshaking, the sense switches, the data-rate generator, and the UART. All four subsections can be independently controlled in software by reading and writing to the appropriate port address.

The sense switches, for instance, are merely a convenience. It is a way for the user to present a frequently used combination of options. These switches, outlined in figure 6, allow selection of data rate, word length, parity condition, and number of stop bits. There is, however, no physical connection between these switches and the other sections. The softwaredriver routine coordinates the option selection.

First the routine determines the state of the switches by reading input port E9. It determines from the setting of switches SW6 thru SW8 what data rate the user wants. The particular code for that rate, selected from table 4, is written to output port E9. The remaining switch settings are written into the UART control register EA. Three bits of this output (b₀ thru b₂) and input port E8 are used for the RS-232C handshaking. The data-rate generator is presented in figure 7.

The sense switches are not absolutely necessary for operation of the serial interface. Most software drivers, such as the ST80 program written by Lance Micklus, offer a selection of the options through the keyboard. Separate data rates for the

Text continued on page 54

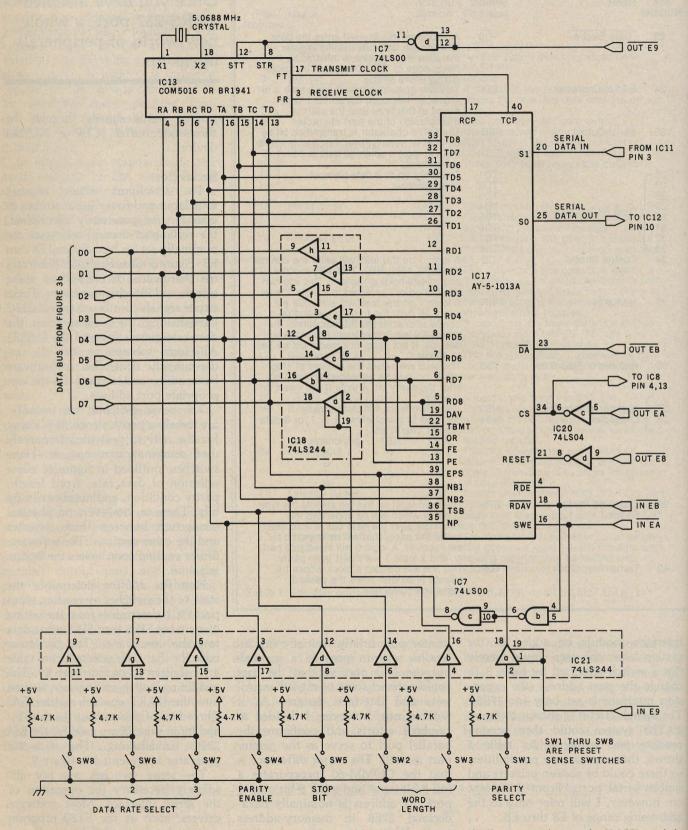


Figure 3a: Section of schematic diagram of COMM-80 interface circuit. Shown here are the data-rate selector, the UART, and the option-selecting switches. The data-rate selector can be either a COM5016 or a BR1941. Various UARTs can be used instead of the AY-5-1013A, including the TR1602, COM2017, S1883, and TMS6011. A UART that uses a single +5 V power supply, such as the AY-3-1015, may also be substituted.

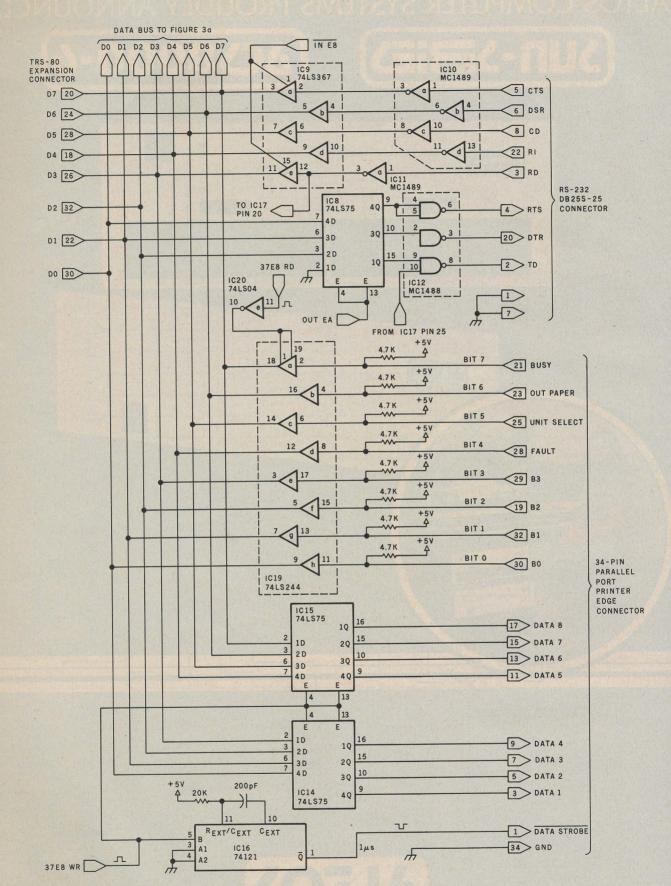


Figure 3b: Section of schematic diagram of COMM-80 interface. Connections to data buses and peripheral connectors are presented here. Some care must be exercised in connecting the COMM-80 to the expansion bus. It is best to use shielded ribbon cable. The production version of the COMM-80 includes two auxiliary expansion-bus edge connectors, which are like the one on the back of the keyboard/processor unit.

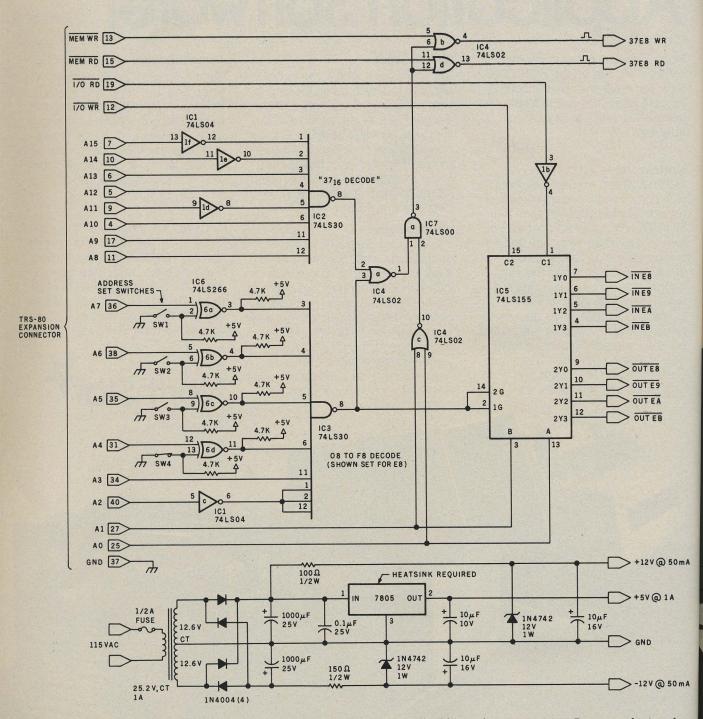


Figure 3c: Section of COMM-80 interface circuit, including power supply and address-selection circuitry. Power to the interface should not be cut off while the TRS-80 is in operation, lest programs be lost. Both units should be powered up and down simultaneously.

Text continued from page 49:


transmitter and receiver can also be established. This is easily accomplished by a direct output command to the data-rate generator using the codes from figure 6. From this point on, serial communication proceeds by simply loading the UART with the data to be transmitted (using the Z80 instruction OUT EB) and reading the UART status register to see if the byte has

been completely sent or if there is a received data word available (with the IN EA instruction).

The software driver needed for this interface is too long to discuss in this

Text continued on page 58

Hire a fast thinker.

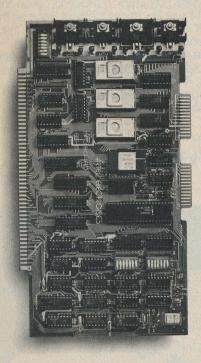


5 MHz CPU Card

■ Intel 8085A-2 microprocessor ■ Hardware floating point ■ Performs calculations six times faster than other CPUs ■ On-board monitor in PROM ■ 1K RAM scratch pad ■ Keyboard or RS232C terminal ■ Variable clock frequency

PRICE—\$850 (California residents add 6% sales tax)

Call or write Artec for details.

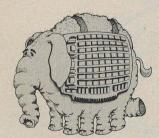

ARTEC ELECTRONICS, INC

605 Old County Rd., San Carlos, CA 94070 Telephone (415) 592-2740

۰		
	Pin 1	PGND — Protective Ground
		This is chassis or equipment ground. It may also be tied to signal ground.
	Pin 2	TD — Transmit Data This is the serial data from the terminal to the remote receiving equip-
		ment. When no data is being sent it is in a marking (1) condition.
	Pin 3	RD — Receive Data This is the serial data from the remote equipment which is transmitted
	Pin 4	to the terminal. RTS — Request to Send
	FIII 4	Controls the direction of data transmission.
		In full-duplex operation an "on" sets transmit mode and an "off" sets non-transmit mode.
		In half-duplex operation an "on" inhibits the receive mode and an "off"
	Pin 5	enables it. CTS — Clear to Send
	11110	Signal from the modem to the terminal indicating ability to transmit
	Pin 6	data. An "on" is "Ready" and an "off" is "not ready." DSR — Data Set Ready
		Signal from the modem to the terminal. An "on" condition indicates that
	Pin 7	the modem is ready. SGND — Signal Ground
	Pin 8	CD — Carrier Detect
		An "on" indicates reception of a carrier from the remote data set; "off" indicates no carrier is being received.
	Pin 20	DTR — Data Terminal Ready: "on" connects the communication equipment to the communications channel; "off" disconnects the com-
		munications equipment from the communications channel.
	Pin 22	RI — Ring Indicator An "on" indicates that a ringing signal is being received on the com-
		munications channel.

Table 2: Designations of pins on the DB-25 connector when used for communication with an RS-232C interface system and description of corresponding signals.

Address Range	SW1	SW2	SW3	SW4
08 thru 0B 18 thru 1B 28 thru 2B 38 thru 3B 48 thru 4B 58 thru 5B 68 thru 6B 78 thru 7B 88 thru 8B 98 thru 9B A8 thru AB B8 thru BB C8 thru CB D8 thru DB E8 thru EB	Closed Closed Closed Closed Closed Closed Closed Closed Open Open Open Open Open Open Open Open	Closed Closed Closed Open Open Open Open Closed Closed Closed Closed Open Open Open	Closed Closed Open Open Closed Open Open Closed Closed Closed Open Closed Open Open Closed Open Open Open Closed Open Open Open Open Closed Open	Closed Open Closed
F8 thru FB	Open	Open	Open	Open

Table 3: Use of the switch-selectable address decoder allows the I/O address range to be varied over the range shown here according to the switch positions specified. (See figure 4.) Radio Shack software uses the address range hexadecimal E8 thru EB.

Listing 1: Part of the output generated during a timesharing session on the Source, in which the TRS-80 equipped with the COMM-80 and a modem was used as a terminal. The Source is a service of the Source Telecomputing Corporation of McLean, Virginia. The hard copy was produced by an LA36 DECwriter connected to the TRS-80 through the COMM-80.

>DATA SYSCOM

COMMAND DESCRIPTION

BASIC CHAT CRTLST PROGRAM IN THE BASIC LANGUAGE.
TALK TO ANOTHER USER ON THE SYSTEM.
DISPLAYS THE CONTENTS OF A FILE, STOPPING EVERY 24
LINES TO GIVE YOU TIME TO CATCH UP. (TYPING A RETURN
RESTARTS THE DISPLAY.)

Listing 1 continued on page 58

				3.	
I ic	tino	1	con	tini	red:

FD

USAGE

STIATA UPI

LISITING I	continuen.		- Van		P.P. C. C. C. A. MC	ANITO	TIATA	DACEC
TIATA	DISPLAY	S CERTAIN	TCA	TTRKWKA	PRUURAMS	HIATI	THIL	DHOLO

GIVES TIME AND DATE.

DATE DELETES A FILE. DEL

AUTOMATICALLY DELAYS OUTPUT TO PRINTING TERMINALS DELAY

WITH SLOWLY RETURNING CARRIAGES.

TEXT EDITOR . TYPE IN A FILE

ENTER FRINTS THE NAME OF ALL YOUR FILES. FILES

COMPILES A FORTRAN PROGRAM. FORTRN SYSTEM SIGN-ON COMMAND.

DISPLAYS CERTAIN OTHER LIBRARY PROGRAMS AND DATA BASES. INFO

LOADS A FORTRAN PROGRAM. LOAD

INVOKES THE ELECTRONIC MAIL PROGRAM. MAIL

SORTS A FILE. NSORT

SIGNS A USER OFF THE SYSTEM. OFF

PLAYS COMPUTER GAMES PLAY

INVOKES THE CLASSIFIED AD/BULLETIN BOARD PROGRAM. POST

RUNS A LIBRARY PROGRAM.

DISPLAYS THE TIME USED FOR THE CURRENT SESSION. TIME

RUNS A LOADED FORTRAN PROGRAM. RUN

LIKE CRTLST, BUT DOES NOT STOP AFTER 24 LINES.

SUMMARY OF YOUR SYSTEM USAGE THIS MONTH.

NOTE: A COMPLETE LIST OF SYSTEM DOCUMENTATION AND PROGRAMMING MANUALS MAY BE VIEWED BY TYPING DATA SYSDOC.

>ONLINE CL0158 TCA422 TCA743 TCD106 TCD419 TCE129	CL0619 TCA434 TCA766 TCD140 TCD437 TCE201	TCA056 TCA516 TCA530 TCD202 TCD444 TCE217	TCA088 TCA569 TCA914 TCI248 TCI2459 TCE274	TCA088 TCA575 TCB419 TCD390 TCD460 TCE317	TCA290 TCA612 TCD011 TCD419 TCE052
---	--	--	---	--	--

1) TO ACCESS THE UPI DATANEWS SYSTEM, SIMPLY TYPE "UPI" AND PRESS "RETURN" .

2) THEN SELECT "NATIONAL", "REGIONAL" OR "STATE" NEWS OR "FEATURES". INCLUDES MOST MAJOR NEWS SYNDICATES (NEW YORK TIMES, UNITED FEATURES, ETC.) AS WELL AS SYNDICATED COLUMNISTS. FOR A COMPLETE LIST OF FEATURES, INDEXED BY LOGICAL CONTENT, RETURN TO THE "COMMAND" LEVEL, AND TYPE.....

3) SELECT FROM THE "GENERAL", "BUSINESS" OR "SPORTS" CATEGORIES; THE SYSTEM WILL THEN ASK YOU FOR ONE OR MORE "KEYWORDS".

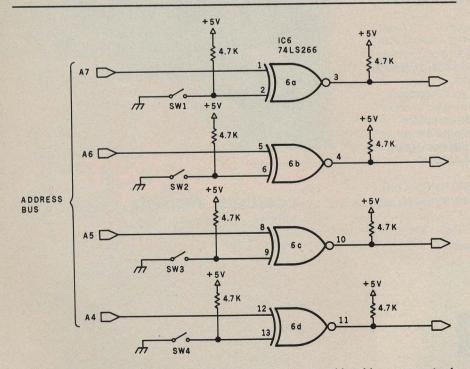


Figure 4: By closing the proper switches, one of sixteen possible address ranges in the I/O-address space can easily be selected. The switches are optional; the desired address range may be hardwired. For complete compatibility with standard TRS-80 software, the hexadecimal address range E8 thru EB should be chosen.

T_A R_A	T _B OR	T _c	$T_{\scriptscriptstyle D}$ $R_{\scriptscriptstyle D}$	Data Rate	Clock Frequency
0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1	0 0 1 1 0 0 1 1 1 0 0 1 1 1 0 0 1 1 1	0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1 1 1 1 1	0 0 0 0 0 0 0 0 0 1 1 1 1 1 1	50 75 110 134.5 150 300 600 1200 200 2400 3600 4800 7200 9600 19200	800 Hz 1200 Hz 1760 Hz 2152 Hz 2400 Hz 4800 Hz 9600 Hz 19.2 kHz 32.08 kHz 32.08 kHz 57.6 kHz 76.8 kHz 115.2 kHz 153.6 kHz 316.8 kHz

Table 4: Chart to select data rates for the COM5016 data-rate generator. Transmission and reception rates may be set independently, according to the parameters specified here.

Text continued from page 54:

article. Also, since this interface is software-compatible with existing TRS-80 hardware, there is no need to write your own driver routine. There are many sources, including the one listed with this article.

Using the COMM-80

Once you have an RS-232C port installed in your computer, a whole new world of peripherals opens up. The electronics industry has been turning out thousands of printers each year which use the RS-232C interface. For example, if you are interested in word processing, then you can attach a high-quality daisywheel printer to your TRS-80. Certain peripherals require a 20 mA current-loop interface; the required circuit is demonstrated in figure 8.

The most obvious application for the COMM-80 is to transform the TRS-80 from a mild-mannered personal computer into a full-fledged computer terminal. Photo 3 shows the system connected to a modem in actual use on the Source timesharing system. Listing 1 is a printout (from an LA36 DECwriter II also connected to the same serial interface) of typical user interaction on this national computer timesharing network. A look at

Text continued on page 62

SEE CORVUS HIGH PERFORMANCE SELECTED DEALERS

ARIZONA Computerland Phoenix 602/956-5727 CALIFORNIA

Computer Place Carmel 408/624-7111 Computers Are Fun Los Angeles 213/475-0566 Computer Merchant San Diego 714/583-3963

Computerland San Francisco 415/546-1592 Computer Emporium San Jose 408/227-5414 Computer Plus

San Jose 408/735-1199 Computer City Santa Ana 714/549-7749 The Computer Store Santa Monica 213/451-0713

Future World Stockton 209/952-2028 COLORADO

Colorado Computer Systems Westminster 303/426-5880 CONNECTICUT

The Computer Store Stamford 203/356-1920 DELAWARE

Computerland Newark 302/738-9656 FLORIDA

Computer Village Miami 305/266-5965 **Gulf Coast Computer** Milton 904/994-8506

GEORGIA Advanced Computer Atlanta 404/255-8984

ILLINOIS Farnsworth Computer Aurora 372/851-3888 Computer Room Chicago312/337-6744 Capital Computer Systems Springfield 217/544-4108

INDIANA Digital Technology Lafayette 317/423-2548

LOUISIANA Microcomputers New Orleans 504/821-0870

MASSACHUSETTS The Computer Store Cambridge 617/354-4599

MINNESOTA Personal Business Systems

Minneapolis 612/929-4120 MISSOURI Computer Country Florissant 314/921-4433

Computers—ASP Kansas City 816/741-8013 **NEBRASKA**

Computerland Omaha 402/391-6716

NEW JERSEY Computer Encounters Princeton 609/924-8757 NEW MEXICO

South West Computer Las Cruces 505/526-2842

NEW YORK

Byte Shop East Levittown 516/731-8116 Computer Factory New York 212/687-5001 McGraw-Hil New York 212/997-4100 Computer Store Rochester 716/244-5000

NORTH CAROLINA

Standard Computers Charlotte 704/399-0228 Byte Shop Raleigh 919/833-0210 OHIO

Byte Ohio Fairfield Park 216/333-3261 OREGON

Computer Emporium Portland 503/228-5242

SOUTH CAROLINA Byte Shop Columbia 803/771-7824

TEXAS

Computer Center Amarillo 806/355-5618 Compushop Dallas 214/234-3412 **KA Computer Store** Dallas 214/634-7870 **Computer Solutions** San Antonio 512/341-8851

UTAH Inkley's Salt Lake City 801/486-3921

VIRGINIA The Computer Place Roanoke 702/982-3661

Home Computer Center Virginia Beach 804/340-1977 WASHINGTON

Computerland Store Federal Way 206/927-8585 WISCONSIN

Blue Lake Computer Madison 608/257-4424

INTERNATIONAL CANADA

Corvus of Canada 705/474-5823 **GREAT BRITAIN**

Keen Computers 602/583254

FRANCE Micrologie

331/6085560 Sonotec 331/610942 MEXICO

Electronica MYMSA 904/584-2347 **WEST GERMANY**

Basis D 0251/77023 MM Computer 08051/4523

CORVUS SYSTEMS, Inc.

2029 O'Toole Ave, San Jose California 95131 (408) 246-0461

World leader in Winchester disk systems, Winchester backups, and other intelligent peripherals.

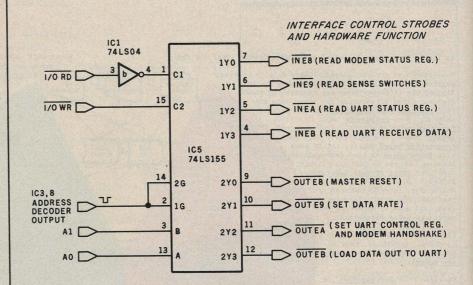


Figure 5: Detail figure demonstrating interface-control strobes. The address decoder (made up of IC3 and IC6) can be set within the range of hexadecimal 08 to F8. TRS-80 compatibility requires a low address of E8. The output-strobe address notations presented refer only to this setting. Switch settings for other addresses are given in table 3.

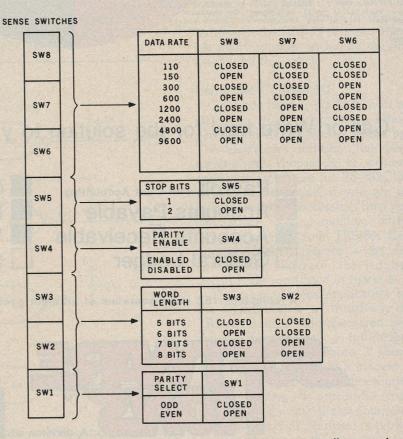


Figure 6: Programmable sense switches are read by the processor to allow preselection of UART options under program control. The correspondence of options and switches is illustrated here.

Table 5: Power supplies needed by the integrated circuits in the COMM-80.

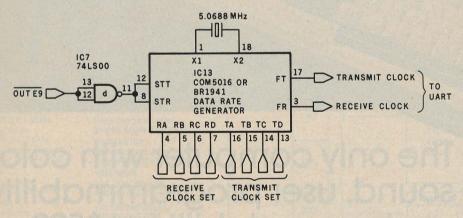


Figure 7: The data-rate generator determines how fast data is sent and received. Transmission and reception rates can be set independently. The specifications for setting up the various possible data rates on the COM5016 are presented in table 4.


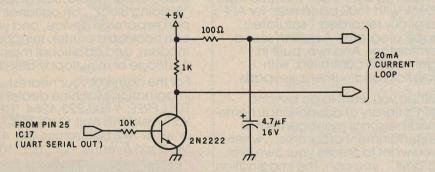


Figure 8: Some peripheral devices (ie: a Teletype ASR33) must be connected by means of a 20 mA current-loop circuit; such a circuit that can be attached to the COMM-80 is shown here.

Text continued from page 58:

some of the capabilities available through these networks might convince some people to use the network's facilities rather than spend thousands of dollars to build up an independent single-user system. At \$2.75 per hour of connect time, it seems a reasonable alternative. For those of you wishing to contact me via the Source, my electronic-mail identification is TCE317. I welcome questions on this or any other topics that I might possibly be able to answer.

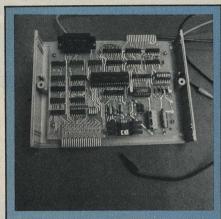

The COMM-80 is available assembled and tested in an attractive 20.95 by 15.24 by 6.35 cm (8.25 by 6 by 2.5 inch) enclosure, including expansion-bus connector and cable, an auxiliary 40-pin expansion-port edge connector, a 34-pin Centronics parallel printer port, RS-232C serial port with DB-25S connector, user's manual, power supply, and terminal software.

Price (including shipping): \$179.95 (New York residents please add appropriate sales tax).

Order from:

The MicroMint Inc 917 Midway Woodmere NY 11595 (516) 374-6793

Next Month

Handheld remote controls for the home-control system as described in the January 1980 Circuit Cellar.